



Department of Electronics and Communication Central University of Rajasthan, Ajmer

SubjectSIGNAL.AND.SYSTEM.....
Subject CodeECE.....
Experiment No.

Name: SHIV KUMAR SINGH

Roll No.:2022BTECE020


Date:

Title: - To prove Maximum power Transfer Theorem using MATLAB

Apparatus required: - Downloaded MATLAB or OCTAVE software in device.

CODE
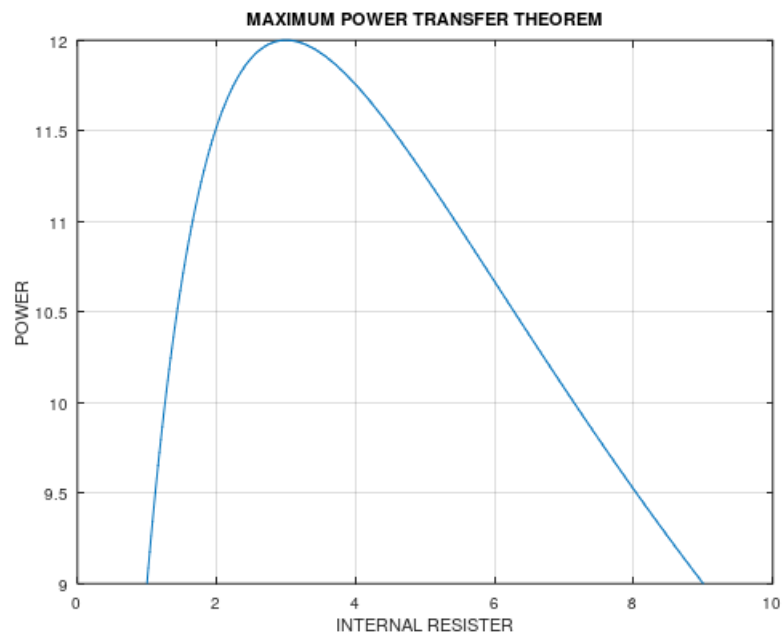
```
1
2 % Maximum power transfer theorem
3 clc
4 close all;
5 clear
6 vth = input("ENTER THE VALUE FOR vth :-");
7 Rin = input("ENTER THE VALUE FOR INTERNAL RESISTOR :-");
8 RL = 1:.02:9;
9 p = (((vth.^2).*RL) ./ (Rin + RL).^2);
10 plot(RL,p);
11 xlabel("INTERNAL RESISTOR");
12 ylabel("POWER");
13 title("MAXIMUM POWER TRANSFER THEOREM");
14 grid;
15
```



Result:-If input voltage is set to be 12 and load resistor is set to be 3 ohm volt then the resultant graph is as under